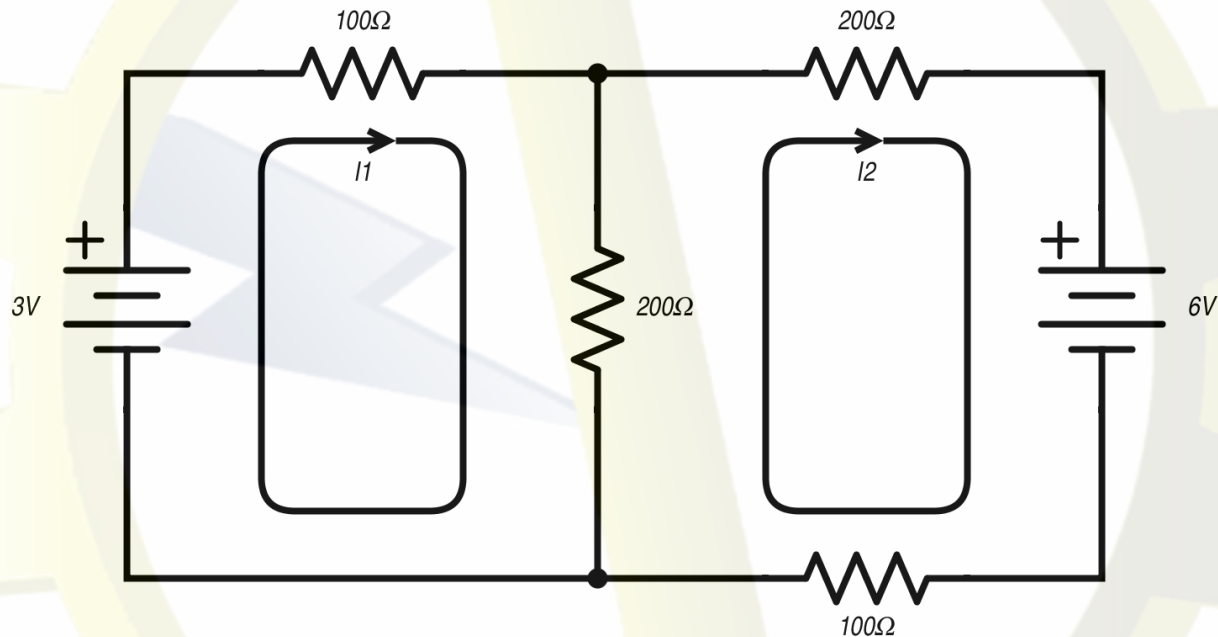


Mesh Analysis and Dependent Sources

Mesh analysis is a very handy tool to compute current within electronic circuits. From knowing the current within each mesh (section), we can solve for voltage and power (watts) at each component. Engineers and designers use this information to select correct parts that won't emit the magic white smoke when power is applied.



We can divide the example above into two meshes, I_1 and I_2 . I_1 designates a virtual current in mesh 1. I_2 shows virtual current in mesh 2. Mesh current flow is usually depicted in a clockwise direction. From here, we write each mesh as a linear equation and use a solving tool to find I_1 and I_2 .

Using Kirchhoff's Voltage Law (KVL), mesh I_1 would be written as:

$$-3 \text{ v} + 100\Omega(I_1) + 200\Omega(I_1 - I_2) = 0 \quad -3 \text{ v} + 100\Omega(I_1) + 200\Omega(I_1 - I_2) = 0$$

The $I_1 - I_2$ is because the current flowing thru the center 200Ω resistor is the difference between the two meshes. Due to the clockwise flow of I_1 , the (-) side of the battery is recorded as the voltage.

This formula can be rewritten as:

$$I_1(300\Omega) - I_2(200\Omega) = 3 \text{ v} \quad I_1(300\Omega) - I_2(200\Omega) = 3 \text{ v}$$

Mesh I_2 can be described in electrical terms as:

$$6 \text{ v} + 100\Omega(I_2) + 200\Omega(I_2 - I_1) + 200\Omega(I_2) = 0 \quad 6 \text{ v} + 100\Omega(I_2) + 200\Omega(I_2 - I_1) + 200\Omega(I_2) = 0$$

Simplified and rewritten, this comes out to:

$$-I_1(200\Omega) + I_2(500\Omega) = -6 \text{ v} \quad -I_1(200\Omega) + I_2(500\Omega) = -6 \text{ v}$$

Here is an online linear equation solver (which will make the solving much simpler). To minimize the chance of symbols being misunderstood, it is best to rename I_1 to "a" and I_2 to "b".

The finished query is:

$$300a - 200b = 3 \quad 300a - 200b = 3$$

, [Equation 1]
and,

$$-200a + 500b = -6 \quad -200a + 500b = -6$$

[Equation 2]
The answers are:

$$I_1(\text{"a"}) = 31100 \text{ A} \quad I_1(\text{"a"}) = 31100 \text{ A}$$

or

$$2.727 \text{ mA} \quad 2.727 \text{ mA}$$

,
and,

$$I_2(\text{"b"}) = -3275 \text{ A} \quad I_2(\text{"b"}) = -3275 \text{ A}$$


or

$$-10.909 \text{ mA} \quad -10.909 \text{ mA}$$

Remember that the current in the center $200\text{-}\Omega$ resistor is $(I_1 - I_2)$. So,

$$2.727 \text{ mA} - (-10.909 \text{ mA}) = 13.636 \text{ mA} \quad 2.727 \text{ mA} - (-10.909 \text{ mA}) = 13.636 \text{ mA}$$

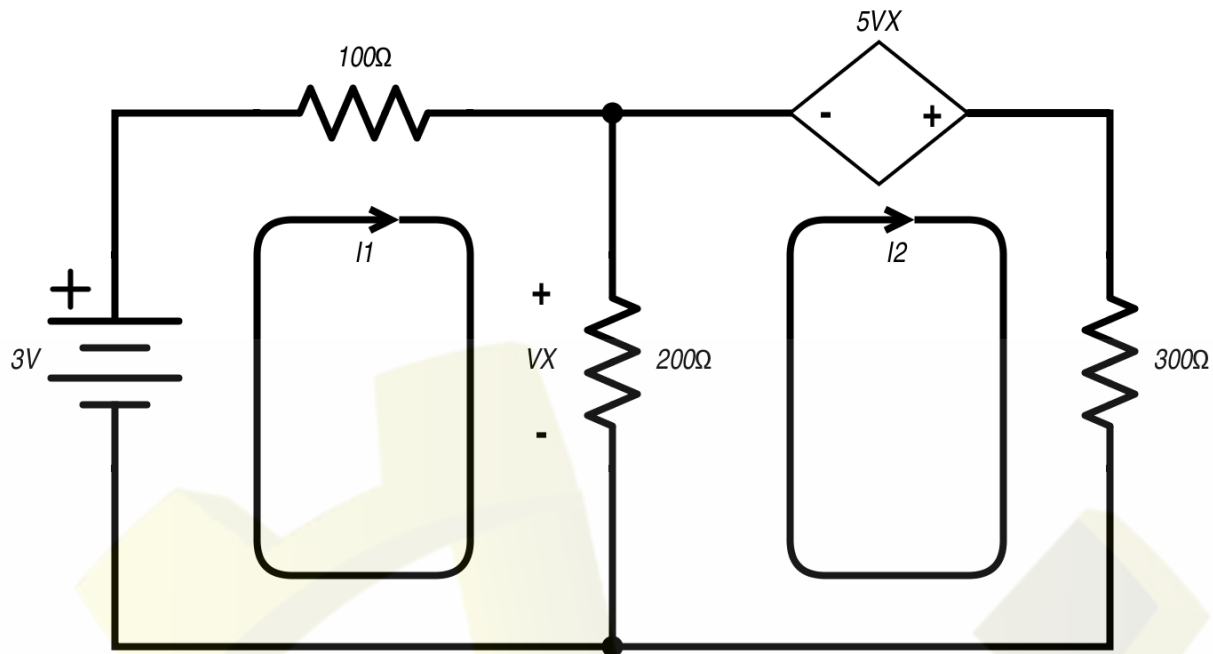The batteries would be considered as an independent voltage source. What would happen if we replaced one of them with a voltage controlled voltage source (VCVS), such as a vacuum tube or FET circuit?



The formula for the I_1 mesh would be identical to the previous example.

It is:

$$I_1(300\Omega) - I_2(200\Omega) = 3 \text{ v} \quad I_1(300\Omega) - I_2(200\Omega) = 3 \text{ v}$$

or for the solver:

$$300a - 200b = 3 \quad 300a - 200b = 3$$

[Equation 3]

Mesh I_2 contains the VCVS dependent voltage source. The gain is noted by the $5V_X$ and the source of the control voltage is seen as the nodes on each side of the center resistor. The formula for I_2 is no more complicated than it is for I_1 .

Starting at the 200- Ω resistor and using KVL we have:

$$200\Omega(I_2 - I_1) - 5V_X + 300\Omega(I_2) = 0 \quad 200\Omega(I_2 - I_1) - 5V_X + 300\Omega(I_2) = 0$$

In a more usable and condensed form, the equation is:

$$-I_1(200\Omega) + I_2(500\Omega) = 5V_X \quad -I_1(200\Omega) + I_2(500\Omega) = 5V_X$$

[Equation 4]

The dependent voltage source is a ratio and not a fixed number at this point. To be able to solve this system, we need to write the formula for V_X . This is found multiplying the resistance 200 Ω by the current.

Since this resistor is used by both meshes, the current is:

$$I_1 - I_2 = I_2$$

V_X is:

$$200\Omega(I_1 - I_2) = 200\Omega(I_1 - I_2)$$

[Equation 5]

V_X will be annotated as “c” for the solver.

Putting the three linear equations (Equations 3, 4 and 5) into a Wolfram Alpha friendly syntax, we have:

$$300a - 200b = 3$$

$$-200a + 500b = 5c$$

$$c = 200(a - b)$$

The results of the equation are: **I_1 has a current of 21.429 mA, I_2 has a current of 17.143 mA, and V_X has a voltage of 0.857 Volts.** Our dependent source has a gain of 5 and therefore is producing 4.286 Volts. At this point someone is thinking “Hey, wait a minute. Why does I_1 have more current in the second example if the dependent source’s voltage is lower than the battery it replaced?” Nice catch! We swapped the polarity for the dependent source and both I_1 and I_2 currents jumped. Hopefully this was planned and our circuit isn’t smoking like a sock in the toaster.

Other dependent sources include Current Controlled Voltage Sources (CCVS), Voltage Controlled Current Sources (VCCS), and Current Controlled Current Sources (CCCS). A bipolar junction transistor is a good example of a CCCS.

The comprehension of mesh analysis with dependent sources is important when planning circuits that utilize amplifiers or amplifying components. The methods are nearly the same as without dependent sources except that more information needs to be presented to achieve a solution.